

# DIGITAL CLOCK USING SEVEN SEGMENT DISPLAY

**DESCRIPTION OF THE PROJECT:** 

 

 

PIN	FUNCTION	
SW0	Reset	Sets clock to 00:00:00
SW1	Mode Change	Allows setting time
SW2	Set Hours	
SW3	Set Minutes	
SW4	Toggle 12-24 hour mode	High-12hr ,Low-24 hr
SW5	Switch Time Zone	High-IST,Low-GMT+3:30

This project involves implementing a digital clock using Verilog on an FPGA-DE10 board. The clock employs a 50 MHz input clock to manage real-time hours, minutes, and seconds, with the output displayed on 7-segment displays. Key features include a time-setting mode, options for 12/24-hour formats, and a +2 hour time zone adjustment with wrap-around support.

## **Key Features:**

## 1. Real-Time Clock Functionality:

- o Utilizes the 50 MHz system clock to generate a 1-second pulse.
- o Tracks seconds, minutes, and hours, handling time wrap-around

# 2. Time Settings:

- Time Setting Mode: A switch allows the user to enter time-setting mode, where
  physical buttons can increment hours and minutes manually.
- o **12/24 Hour Mode**: A toggle switch allows switching between 12-hour and 24-hour formats, correctly managing midnight (0:00) and noon (12:00).

### 3. Time Zone Adjustment:

- An additional switch facilitates a +2 hour time zone adjustment. For instance, if the current time is set to Iran's time zone (GMT +3:30), activating the +2 hour adjustment will shift the time to India's time zone (GMT +5:30 (IST)).
- This change includes automatic wrap-around (e.g., 23:00 in Iran's time would become 01:00 in India's time).

# 4. Display System:

- o Utilizes six 7-segment displays for hours, minutes, and seconds
- A decoder function translates binary-coded time digits into 7-segment signals, ensuring readability

## 5. Efficient Timekeeping:

- A clock divider converts the 50 MHz input clock to a 1 Hz pulse, ensuring accurate time increments.
- Wrap-around logic is implemented for seconds, minutes, and hours to ensure the clock's continuous and reliable operation


#### **VERILOG CODE:**


```
module digital_clock(
    input wire clk,
    input wire reset,
    input wire mode_switch,
    input wire button_hours,
    input wire button_minutes,
    input wire hour_mode_switch,
    input wire time_zone_switch,
    output reg [6:0] seg0, output reg [6:0] seg1,
    output reg [6:0] seg2,
    output reg [6:0] seg3, output reg [6:0] seg4,
    output reg [6:0] seg5
);
    parameter DIVISOR = 50000000;
    reg [25:0] clk_divider = 0;
    reg one_sec_pulse = 0;
    reg [5:0] seconds = 0;
reg [5:0] minutes = 0;
    reg [4:0] hours = 0;
   // Time setting
   always @(posedge clk or posedge reset) begin
        if (reset) begin
             hours \leftarrow 0;
             minutes <= 0;
             seconds <= 0;
        end else if (mode_switch) begin
             // Time Setting Mode
if (button_hours) begin
                  if (hours == 23)
                       hours \leftarrow 0;
                  else
                       hours <= hours + 1;
             end
             if (button_minutes) begin
                  if (minutes == 59)
                      minutes <= 0;
                       minutes <= minutes + 1;</pre>
             end
        end
        else if (one_sec_pulse) begin
             // Normal clock operation
if (seconds == 59) begin
                  seconds <= 0;
                  if (minutes == 59) begin
                       minutes <= 0;
                       if (hours == 23)
                            hours \leftarrow 0;
                       else
                           hours <= hours + 1;
                  end else begin
                       minutes <= minutes + 1;
                  end
             end else begin
                  seconds <= seconds + 1;
             end
        end
   end
```

```
// Time Zone Adjustment
       wire [4:0] adjusted_hours;
       assign adjusted_hours = (time_zone_switch) ? ((hours + 2) % 24) : hours;
       // 12/24 Hour Mode Switch
wire [4:0] display_hours;
       adjusted_hours;
       // 7-Segment Display Decoder
       function [6:0] seven_segment_decoder;
   input [3:0] digit;
             input [3:0] digit;
case (digit)
   4'd0: seven_segment_decoder = 7'b1000000;
   4'd1: seven_segment_decoder = 7'b1111001;
   4'd2: seven_segment_decoder = 7'b0100100;
   4'd3: seven_segment_decoder = 7'b0110000;
   4'd4: seven_segment_decoder = 7'b0011001;
   4'd5: seven_segment_decoder = 7'b0010010;
   4'd6: seven_segment_decoder = 7'b0010010;
   4'd7: seven_segment_decoder = 7'b1111000;
   4'd8: seven_segment_decoder = 7'b00000000;
   4'd9: seven_segment_decoder = 7'b0010000;
   default: seven_segment_decoder = 7'b11111111;
endcase
              endcase
       endfunction
       always @(*) begin
              seg0 = seven_segment_decoder(seconds % 10);
              seg1 = seven_segment_decoder(seconds / 10);
             seg2 = seven_segment_decoder(minutes % 10);
seg3 = seven_segment_decoder(minutes / 10);
              seg4 = seven_segment_decoder(display_hours % 10);
              seg5 = seven_segment_decoder(display_hours / 10);
       end
endmodule
```

### **RTL VIEW:**

(zoomed out)

 

 

(zoomed in - input side)

#### **VIDEO LINKS:**

- 1. First Iteration
- 2. Mode Change Time Setting Buttons
- 3. Checking if Time is Incrementing Properly After Setting 11:59
- 4. Time Change Can Only Be Made When Mode Change Switch is High
- 5. Added 12-24 Hour Functionality
- 6. Another 24-12 Hour Video
- 7. Time Zone and Overall Video
- 8. Verilog code drive link Click here to view the file